
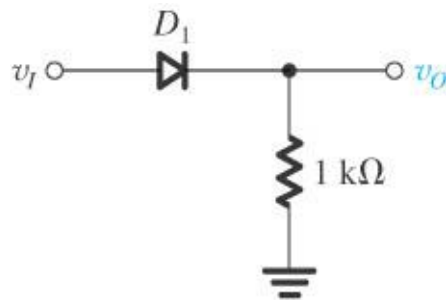

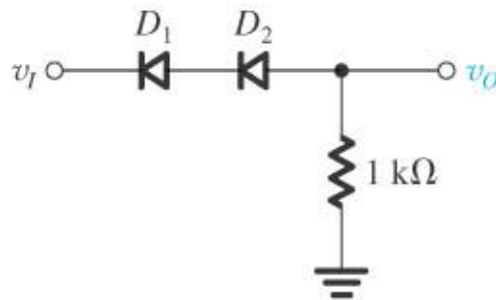
# Exercices


- Ideal diode with  $V_T = 0$  V
- $v_I$  is a 10-V peak sine wave
- $v_O$  ?



(a)



(b)


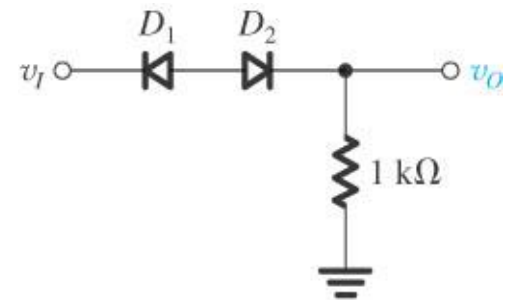


(c)

# Exercices
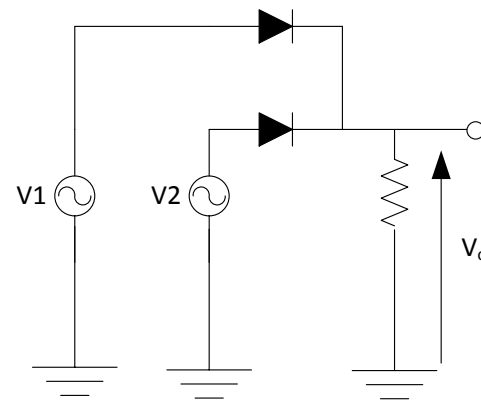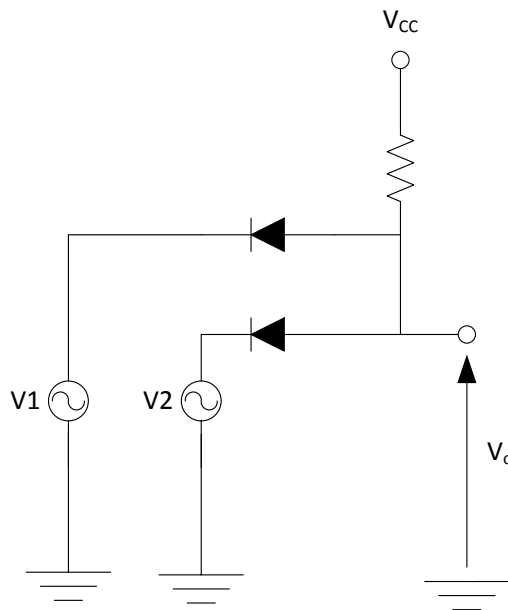
## Logic functions


- Assume diodes perfect ( $V_T = 0$ )
- $V_1$  and  $V_2$  can be equal to 0 or  $V_{CC}$
- $V_o(V_1, V_2)$  ?
- Which logic functions are implemented in both cases ?



# Exercices
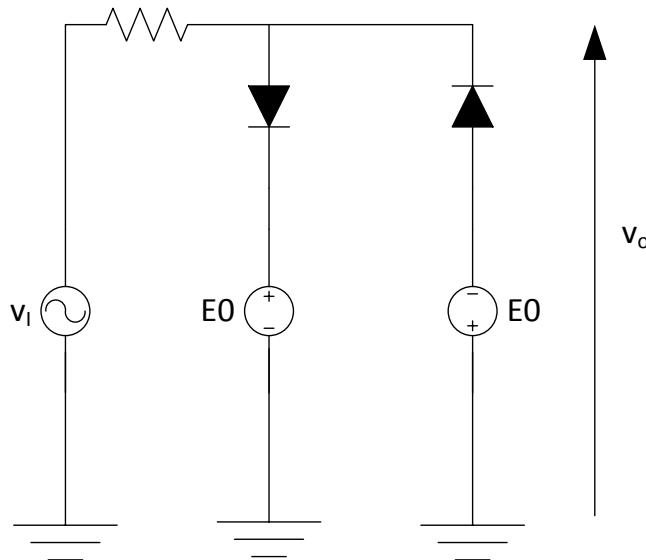
## Clamping circuit


- Ideal diode with  $V_T = 0.7 \text{ V}$
- $v_I$  is a 10-V peak sine wave and  $E_0 = 5 \text{ V}$
- $v_O$  ?



# Exercices
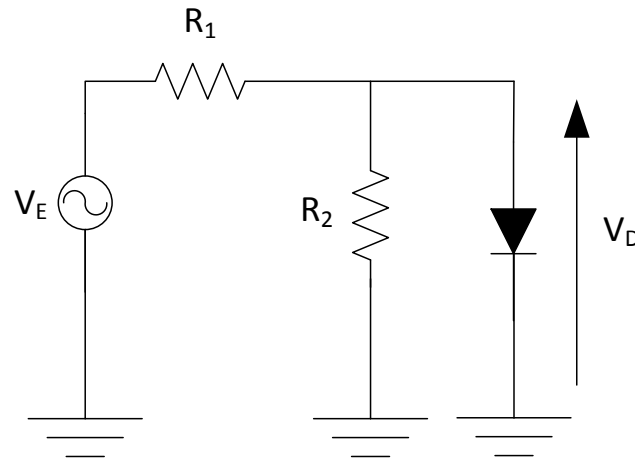
## Voltage limiter


- Assume diode ideal with  $V_T = 0.7 \text{ V}$
- For what value of  $V_E$  is diode blocking/passing
- For both cases, compute  $i_{R1}$ ,  $i_{R2}$  and  $V_D$



# Exercices

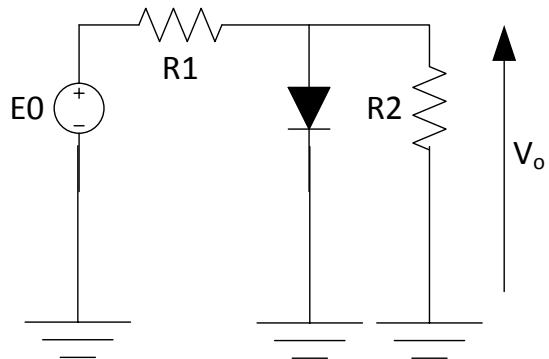**E0=5, R1=180, R2=150**

- Diode characteristic  $i = I_S e^{v/V_T}$  with
  - $I_S = 7.10^{-15} \text{ A}$
  - $V_T = 25 \text{ mV}$
- $V_o$  if R2 connected ?
- $V_o$  if R2 not connected (graphically) ?



# Exercices

- Two imperfect diodes
- What are the values of  $i_{D1}$ ,  $i_{D2}$ ,  $i_R$  and  $v_o$  (graphically)?

