


## Chapter 4 : Single-stage MOS amplifiers - exercices

### BIASING IN MOS AMPLIFIER CIRCUITS
 
#### Exercise 1 (D4.55)

Consider the classical biasing circuit shown in the figure, using a 15-V supply. For the NMOS,  $V_t = 1.2\text{ V}$ ,  $\lambda = 0$ ,  $\frac{k'_n W}{L} = 3200\ \mu\text{A}/\text{V}^2$ . Arrange that the drain current is  $2\text{ mA}$ , with one-third of the supply voltage across each of  $R_S$  and  $R_D$ . Use  $22\text{ M}\Omega$  for the larger of  $R_{G1}$  and  $R_{G2}$ .


- What are the values of  $R_{G1}$ ,  $R_{G2}$ ,  $R_S$  and  $R_D$ ?
- How far is the drain voltage from the edge of saturation?


 
#### Exercise 2 (D4.56)

Using the circuit topology displayed in the figure, arrange to bias the NMOS transistor at  $I_D = 2\text{ mA}$  with  $V_D$  midway between cutoff and the beginning of the triode operation. The available supplies are  $\pm 15\text{ V}$ . For the NMOS transistor,  $V_t = 0.8\text{ V}$ ,  $\lambda = 0$ ,  $\frac{k'_n W}{L} = 2500\ \mu\text{A}/\text{V}^2$ . Use a gate-bias resistor of  $10\text{ M}\Omega$ .


- What are the values of  $R_S$  and  $R_D$ ?


 
#### Exercise 3 (D4.63)

For the circuit shown in the figure, with  $I = 1\text{ mA}$ ,  $R_G = 0\ \Omega$ ,  $R_D = 5\text{ k}\Omega$  and  $V_{DD} = 10\text{ V}$ , the NMOS transistor has the following characteristics:  $V_t = 1\text{ V}$ ,  $\lambda = 0$ ,  $\frac{k'_n W}{L} = 0.5\text{ mA}/\text{V}^2$ .


- What are the values of  $V_S$ ,  $V_D$  and  $V_{DS}$ ?



#### Exercise 4 (D4.64)

In the circuit of the figure, let  $R_G = 10\text{ M}\Omega$ ,  $R_D = 10\text{ k}\Omega$  and  $V_{DD} = 10\text{ V}$ . The NMOS transistor has  $V_t = 1\text{ V}$ ,  $\lambda = 0$ ,  $\frac{k'_n W}{L} = 0.5\text{ mA/V}^2$ .

 - a) What are the values of  $V_D$  and  $V_G$ ?




#### Exercise 5 (D4.65)

Using the feedback bias arrangement shown in the figure of exercise 4, with a  $9\text{ V}$  supply and an NMOS device for which  $V_t = 1\text{ V}$ ,  $\lambda = 0$ ,  $\frac{k'_n W}{L} = 0.4\text{ mA/V}^2$ , find  $R_D$  to establish a drain current of  $2\text{ mA}$ .

#### Exercise 6 (D4.66)

The figure shows a variation of the feedback-bias circuit of the previous exercises. Using a  $6\text{ V}$  supply with an NMOS transistor for which  $V_t = 1.2\text{ V}$ ,  $\lambda = 0$ ,  $\frac{k'_n W}{L} = 3.2\text{ mA/V}^2$ , provide a design which biases the transistor at  $I_D = 2\text{ mA}$ , with  $V_{DS}$  large enough to allow saturation operation for a  $2\text{-V}$  negative signal swing at the drain. Use  $22\text{ M}\Omega$  as the largest resistor in the feedback-bias network.

 - a) What are the values of  $R_{G1}$ ,  $R_{G2}$  and  $R_D$ ?




## SMALL-SIGNAL OPERATION AND MODELS & SINGLE-STAGE MOS AMPLIFIERS
 
### Exercise 7 (D4.69)

Consider the NMOS amplifier of the figure for  $V_t = 2\text{ V}$ ,  $\frac{k'_n W}{L} = 1\text{ mA/V}^2$ ,  $V_{GS} = 4\text{ V}$ ,  $V_{DD} = 10\text{ V}$  and  $R_D = 3.6\text{ k}\Omega$ .


- Find the DC quantities  $I_D$  and  $V_D$
- Calculate the value of  $g_m$  at the bias point
- Calculate the value of the voltage gain
- If the NMOS has  $\lambda = 0.01\text{ V}^{-1}$ , find  $r_o$  at the bias point and calculate the voltage gain.



### Exercise 8 (D4.74)

For the NMOS amplifier in the figure, replace the transistor with its T-equivalent circuit. Derive expressions for the voltage gains


- $v_s/v_i$
- $v_d/v_i$

 
 
### Exercise 9 (D4.75)

In the circuit of the figure, the NMOS transistor has  $V_t = 0.9\text{ V}$  and  $V_A = 50\text{ V}$  and operates with  $V_D = 2\text{ V}$ .


- What is the voltage gain  $v_o/v_i$ ?
- What do  $V_D$  and the gain become if  $I$  is increased to  $1\text{ mA}$ ?


 
### Exercise 10 (D4.77)


The figure shows a discrete-circuit CS amplifier employing the classical biasing circuit we saw in the lecture. The input signal  $v_{sig}$  is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to the ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite).

- If the transistor has  $V_t = 1\text{ V}$ , and  $\frac{k'_n W}{L} = 2\text{ mA/V}^2$ , verify that the biasing circuit establishes  $V_{GS} = 2\text{ V}$ ,  $I_D = 1\text{ mA}$ , and  $V_D = +7.5\text{ V}$ . That is, assume these values and verify that they are consistent with the values of the circuit components and the device parameters.
- Find  $g_m$  and  $r_o$  if  $V_A = 100\text{ V}$
- Draw a complete small-signal equivalent circuit for the amplifier assuming all capacitors behave as short-circuits at signal frequencies
- Find  $R_{in}$ ,  $v_{gs}/v_{sig}$ ,  $v_o/v_{gs}$ , and  $v_o/v_{sig}$


 
### Exercise 11 (D4.82)

A CS amplifier using a NMOS transistor biased in the manner of the figure for which  $g_m = 2\text{ mA/V}$  is found to have an overall voltage gain  $A_v = -16$ . What value of resistance  $R_S$  inserted at the source terminal of the NMOS leads to reduce the voltage gain by a factor of 4?



**Exercise 12 (D4.88)**

- a) The NMOS transistor in the source-follower circuit of figure (a) has  $g_m = 5 \text{ mA/V}$  and a large  $r_o$ . Find the open-circuit voltage gain and the output resistance.
- b) The NMOS transistor in the common-gate amplifier of figure (b) has  $g_m = 5 \text{ mA/V}$  and a large  $r_o$ . Find the input resistance and the voltage gain.
- c) If the output of the source-follower in (a) is connected to the input of the common-gate amplifier in (b), use the previous results to obtain the overall voltage gain  $v_o/v_i$

